


Zener Diode

Zener Diode and Avalanche Breakdown

Basics of Zener Voltage Regulator

331

Zener Region

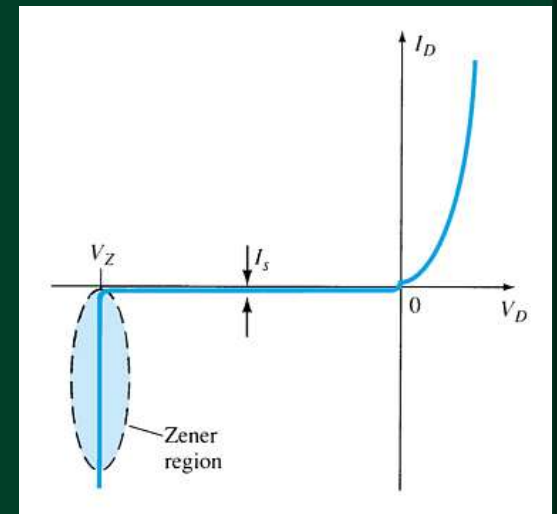

- The Zener region is in the diode's reverse-bias region.
- At some point the reverse bias voltage is so large the diode breaks down and the reverse current increases dramatically.
- The maximum reverse voltage that won't take a diode into the zener region is called the **peak inverse voltage** or **peak reverse voltage**.
- The voltage that causes a diode to enter the zener region of operation is called the **zener voltage (V_Z)**.

332

Zener Diode

- A **Zener diode** is a type of diode specifically designed to operate in the **reverse breakdown region**.
- Unlike ordinary diodes, which are damaged if the reverse voltage exceeds a certain threshold, Zener diodes **are designed to withstand breakdown and maintain a stable reverse voltage**.

333

Zener Diode

- **Key Features of a Zener Diode**

- 1.Reverse Breakdown Operation:**

- 1. The diode allows current to flow in the reverse direction when the reverse voltage reaches a specified level, called the **Zener voltage (V_Z)**.
 - 2. This reverse breakdown does not damage the diode if operated within its power rating.

- 2.Voltage Regulation:**

- 1. The Zener diode maintains a **nearly constant voltage (V_Z)** across its terminals even when the input voltage or load changes, making it useful as a **voltage regulator**.

- 3.Bidirectional Behavior:**

- 1. In forward bias, it behaves like a regular diode.
 - 2. In reverse bias, it exhibits a **sharp breakdown at V_Z** , allowing significant current while holding the voltage constant.

334

Zener Diode

- **Construction and Working**

- **Construction:**

- Zener diodes are heavily doped to create a thin depletion region, enabling the **Zener breakdown mechanism** at low voltages.
 - They can also exhibit **avalanche breakdown** for higher voltage ratings ($>6V$).

- **Working Principle:**

- In forward bias: It behaves like a standard diode.
 - In reverse bias:
 - Below V_Z : Very little reverse current flows.
 - At V_Z : The diode enters breakdown and conducts a high current while maintaining the reverse voltage nearly constant.

335

Zener Diode

- **Applications**

- 1. Voltage Regulation:**

- Zener diodes are used in **power supply circuits** to stabilize voltage by providing a constant reference voltage.

- 2. Overvoltage Protection:**

- Protects sensitive electronic components from voltage spikes by clamping the voltage to V_Z .

- 3. Waveform Clipping:**

- Used to clip signals at a specific voltage, useful in signal processing.

- 4. Voltage Reference:**

- Provides a stable reference voltage for precise applications, like in analog-to-digital converters.

336

Zener Diode

• Characteristics

1. Zener Voltage (V_Z):

- Defined as the reverse voltage at which the diode enters breakdown.
- Can range from a few volts to hundreds of volts.

2. Power Dissipation:

- The maximum power the diode can dissipate, given by $P = V_Z \times I_Z$, where I_Z is the current through the diode.

3. Temperature Dependence:

- The Zener voltage changes with temperature.
- Zener diodes below $\sim 5.6V$ have a negative temperature coefficient, while those above $\sim 5.6V$ have a positive coefficient.

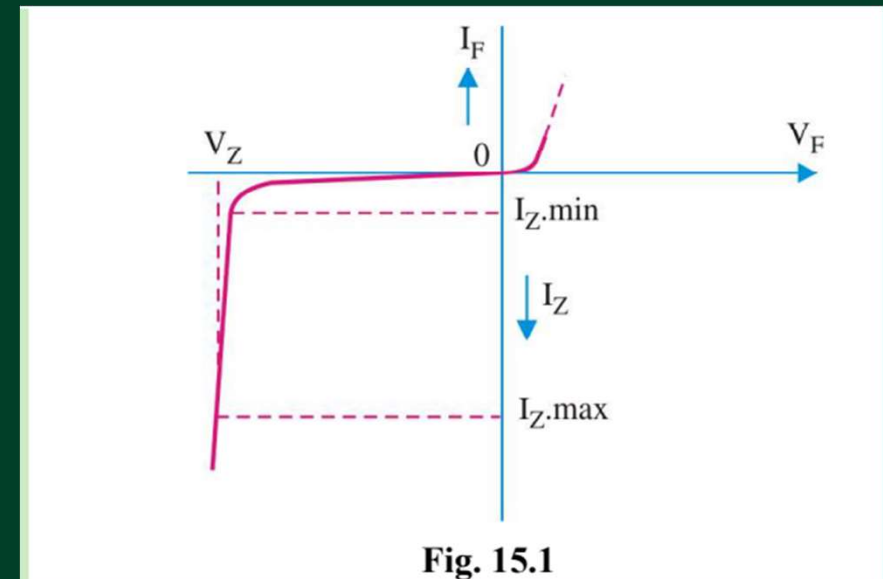


Fig. 15.1

337

Zener Diode


• Example Circuit for Voltage Regulation

• Components:

- Zener diode ($V_Z = 5.6V$)
- Resistor (R)
- Input voltage source (V_{in})

• Operation:

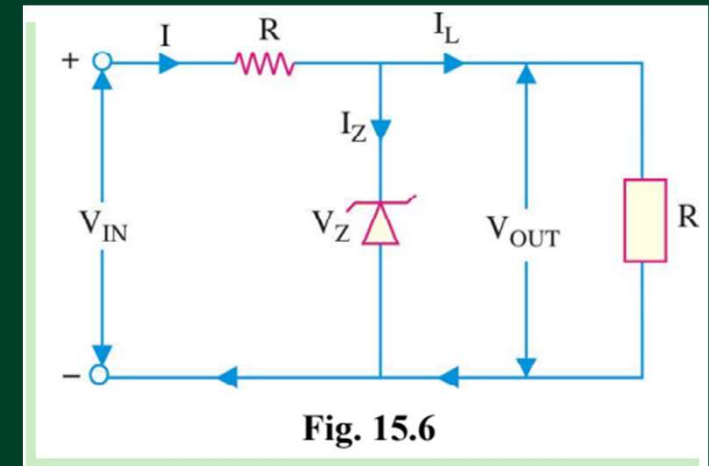1. $V_{in} > V_Z$: The Zener diode breaks down and clamps the voltage across it to V_Z .
 2. The resistor limits the current through the diode to prevent damage.
- This setup ensures a stable output voltage (V_Z) regardless of variations in V_{in} or load conditions.



338

Zener Breakdown

- **Mechanism:**

- Zener breakdown occurs due to quantum mechanical tunneling of electrons across a narrow depletion region in a heavily doped PN junction.
- When the electric field across the junction becomes extremely strong (due to a high reverse voltage), it allows electrons to "tunnel" through the energy barrier.

339

Zener Breakdown

- **Key Features:**

- Happens in **heavily doped diodes** with thin depletion regions.
- Dominates at **low reverse voltages** (typically less than 6V).
- The breakdown voltage (Zener voltage) is well-defined and nearly constant for a given diode.
- No significant damage to the diode if operated within the power ratings.

- **Applications:**

- Used in **Zener diodes** for voltage regulation and reference voltage sources.

340

Avalanche Breakdown

- **Mechanism:**

- Avalanche breakdown occurs due to the impact ionization process.
- In a less heavily doped PN junction, the depletion region is wider.
- High reverse voltage accelerates free electrons, causing them to collide with lattice atoms and generate additional electron-hole pairs.
- This multiplication leads to a large current.

341

Avalanche Breakdown

- **Key Features:**

- Happens in lightly doped diodes with wide depletion regions.
- Occurs at higher reverse voltages (typically above 6V).
- Dependent on temperature, as increased thermal energy aids the ionization process.
- If the current is not limited externally, it can damage the diode.

- **Applications:**

- Used in avalanche diodes for applications requiring high-voltage operation or protection circuits.

342

Zener Vs Avalanche Breakdown

Feature	Zener Breakdown	Avalanche Breakdown
Doping	Heavy	Light
Depletion Region	Narrow	Wide
Voltage Range	Low (<6V)	High (>6V)
Mechanism	Quantum Tunneling	Impact Ionization
Temperature Dependence	Weak	Strong
Damage Risk	Low	High without current limiting


343

Zener Vs Avalanche Breakdown

- **Quantum tunneling** is a quantum mechanical phenomenon that occurs when particles pass through a potential energy barrier that they shouldn't be able to pass through according to classical mechanics.
- **Impact ionization** is a process that occurs in high electric fields when electrons or holes gain enough energy to break a bond and create electron-hole pairs.

344

Zener Experiment Setup

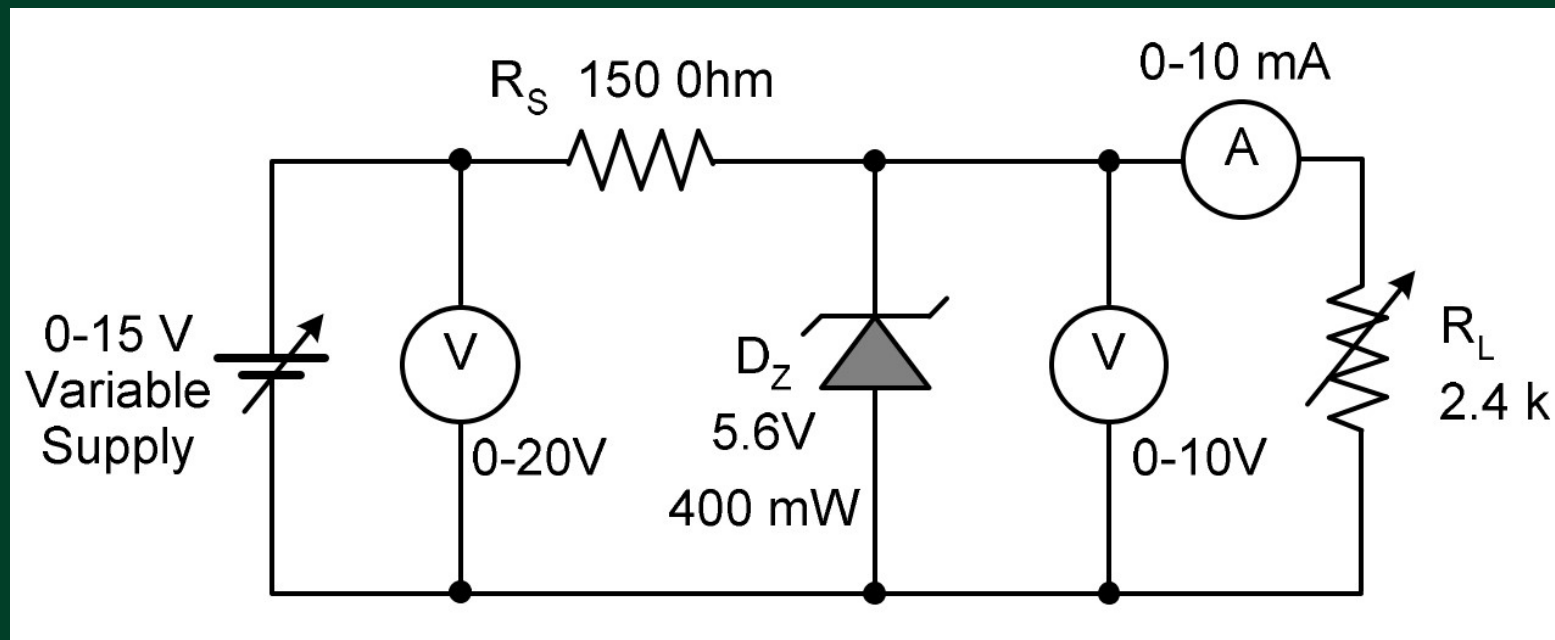

345

Zener Experiment Setup

Output requirements

$$V_o = 5.6V, \quad I_L = 10mA$$

When input is in the range $10 \pm 3V$

Select 5.6V Zener

$$P_o = 0.25W, \quad V_z = 5.6V, \quad I_{zmax} = 45mA, \quad I_{zmin} = 5mA$$

Design of load resistor, R_L

$$R_L = \frac{V_o}{I_{Lmin}}$$

$V_o = V_z$. For a load regulation from 5mA to 15mA, $I_{Lmin} = 5mA$.

$$R_L = \frac{5.6}{5 \times 10^{-3}} = 1.12k\Omega$$

346

Zener Experiment Setup

Design of R_s

$$R_{smin} = \frac{V_{imin} - V_Z}{I_{Lmax} + I_{Zmin}} = \frac{7 - 5.6}{(15 + 5) \times 10^{-3}} = 70\Omega$$

$$R_{smax} = \frac{V_{imax} - V_Z}{I_{Lmin} + I_{Zmax}} = \frac{13 - 5.6}{(5 + 45) \times 10^{-3}} = 148\Omega$$

Take $R_{smin} < R_s < R_{smax}$



$R_s = 120\Omega$

Power dissipation by $R_s = I_{smax}^2 \times R_s = (I_{Lmin} + I_{Zmax})^2 \times R_s = ((5 + 45) \times 10^{-3})^2 \times 120 = 0.3W$

Take $R_s = 120\Omega, 0.5W$

347 Zener Diodes

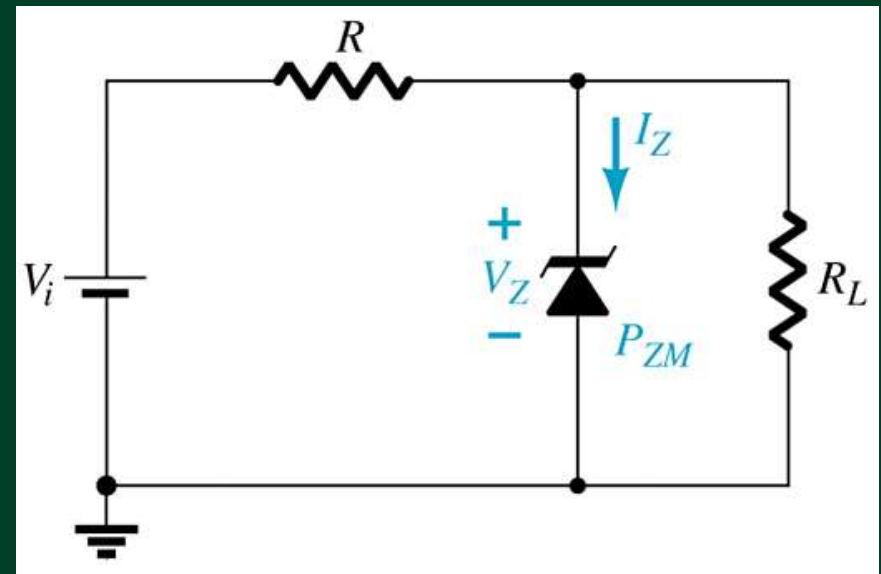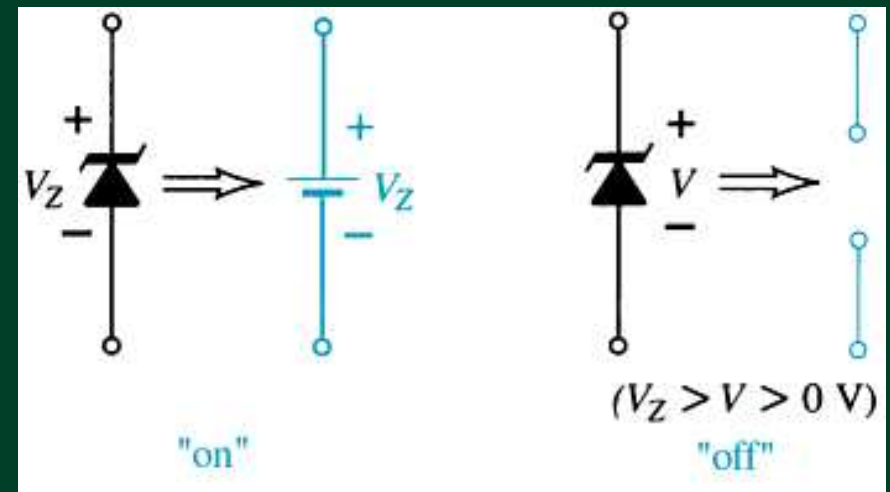- The Zener is a diode operated in reverse bias at the Zener Voltage (V_Z).
- When $V_i \geq V_Z$
 - The Zener is on
 - Voltage across the Zener is V_Z
 - Zener current: $I_Z = I_R - I_{RL}$
 - The Zener Power: $P_Z = V_Z I_Z$
- When $V_i < V_Z$
 - The Zener is off
 - The Zener acts as an open circuit



348


Zener Resistor Values

If R is too large, the Zener diode cannot conduct because the available amount of current is less than the minimum current rating, I_{ZK} . The minimum current is given by:

$$I_{Lmin} = I_R - I_{ZK}$$

The *maximum* value of resistance is:

$$R_{Lmax} = \frac{V_Z}{I_{Lmin}}$$

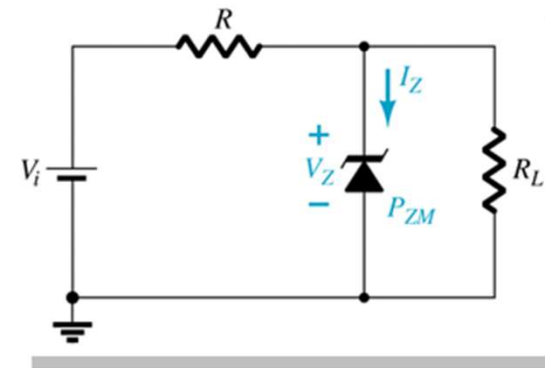

If R is too small, the Zener current exceeds the maximum current rating, I_{ZM} . The maximum current for the circuit is given by:

$$I_{Lmax} = \frac{V_L}{R_L} = \frac{V_Z}{R_{Lmin}}$$

The *minimum* value of resistance is:

$$R_{Lmin} = \frac{RV_Z}{V_i - V_Z}$$

349

Practical Applications

- **Rectifier Circuits**
 - Conversions of AC to DC for DC operated circuits
 - Battery Charging Circuits
- **Simple Diode Circuits**
 - Protective Circuits against
 - Overcurrent
 - Polarity Reversal
 - Currents caused by an inductive kick in a relay circuit
- **Zener Circuits**
 - Overvoltage Protection
 - Setting Reference Voltages