


Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

00EST130121904

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

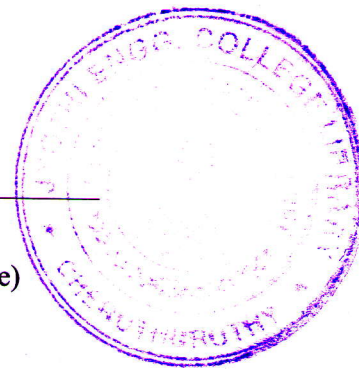Second Semester B.Tech Degree Examination July 2021 (2019 scheme)



Course Code: EST130

Course Name: BASICS OF ELECTRICAL AND ELECTRONICS ENGINEERING  
(2019 Scheme)

**PART I: BASIC ELECTRICAL ENGINEERING**

Max. Marks:50

Duration:90min

**PART A**

*Answer all questions, each carries 4 marks.*

Marks


- 1 A conductor of length 0.5m kept at right angles to a uniform magnetic field of flux density  $2\text{Wb/m}^2$  moves with a velocity of 75 m/s at an angle of  $60^\circ$  to the field. Calculate the emf induced in the conductor. (4)
- 2 Define mutual inductance. Two coupled coils of self inductance 0.8H and 0.35H have a coefficient of coupling 0.9. Find the mutual inductance between the coils. (4)
- 3 State and explain Kirchhoff's laws with examples (4)
- 4 Find the trigonometrical, exponential and polar forms of the vector  $8+j6$ . (4)
- 5 Define (i) active power, (ii) reactive power, (iii) apparent power and (iv) power factor of an ac circuit. (4)

**PART B**

*Answer one full question from each module, each question carries 10 marks*

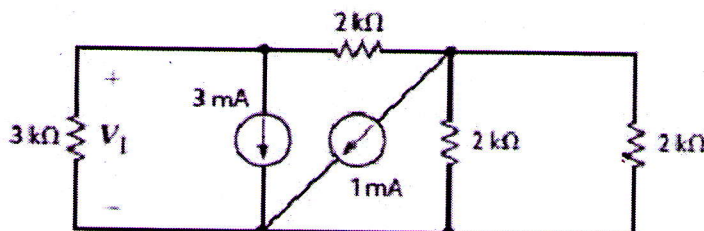**Module-I**


- 6 Use nodal analysis to find  $V_1$  in the given circuit. (10)



**OR**

- 7 Find the current in each branch of the following circuit using mesh analysis? (10)

00EST130121904

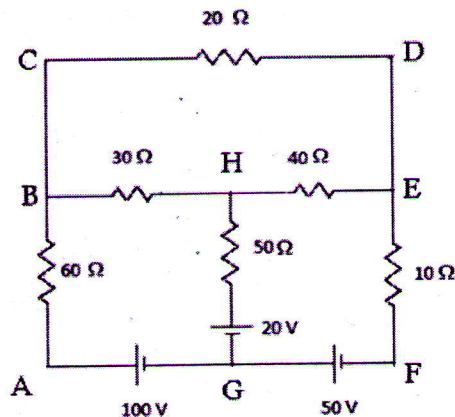


Module-II

- 8 An iron ring of cross sectional area  $1\text{cm}^2$  is wound with a coil of 2000 turns. Calculate the magnetising current required to produce a flux of  $0.1\text{ mWb}$  in the iron path if mean length of the path is  $30\text{cm}$  and relative permeability of iron is 2500. Neglect magnetic leakages and fringing. (10)

OR

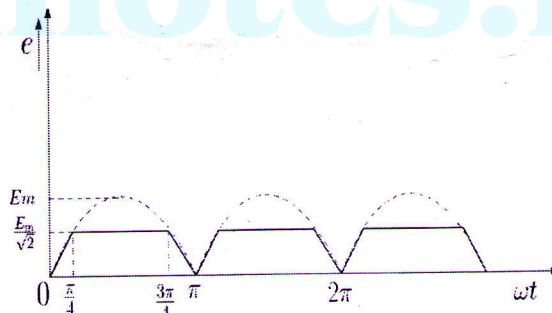- 9 A full wave rectified sine function is clipped at  $0.707$  of its maximum value as shown in figure. Find the average and rms values of the function. (10)



Module-III

- 10 A sinusoidal voltage  $V=230\angle 15^\circ$  of frequency  $50\text{ Hz}$  is applied to a series RL circuit consisting of  $R=5\ \Omega$  and  $L=0.1\text{ H}$ . Calculate (i) rms current and its phase angle (ii) power factor (iii) average power (iv) reactive power and (v) apparent power drawn by the circuit. (10)

OR

- 11 A balanced 3 phase load consists of 3 coils each of resistance  $6\ \Omega$  and inductive reactance of  $8\ \Omega$ . Determine the line current and power absorbed when the coils are (i) star connected (ii) delta connected across  $400\text{V}$ , 3 phase supply. (10)

\*\*\*\*\*

**PART II: BASIC ELECTRONICS ENGINEERING**

Max. Marks: 50

Duration: 90 min

**PART A***Answer all questions, each carries 4 marks.*

Marks

- |    |  |     |
|----|--|-----|
| 12 | In a 4 band resistor the last colour in the colour band is gold. If the upper range of resistance is $3.465\Omega$ find its colour code. | (4) |
| 13 | Differentiate between Avalanche breakdown and Zener breakdown?   | (4) |
| 14 | Draw and explain the block diagram of a public address system.   | (4) |
| 15 | Give reasons for decrease in transistor amplifier gain at low frequencies and high frequencies.  | (4) |
| 16 | Explain the relevance of Intermediate Frequency in a superheterodyne receiver.   | (4) |

**PART B***Answer one full question from each module, each question carries 10 marks***Module-IV**

- |    |  |     |
|----|--|-----|
| 17 | a) What are the different types of inductors? Give two typical applications of inductor. | (5) |
|    | b) Describe the VI characteristics of PN junction diode.                                 | (5) |

**OR**

- |    |   |     |
|----|---|-----|
| 18 | a) Derive the relation between common base current gain and common emitter current gain,        | (4) |
|    | b) Sketch the output characteristic of a transistor and explain different regions of operation. | (6) |

**Module-V**

- |    |   |     |
|----|---|-----|
| 19 | a) Explain the working of a full wave bridge rectifier. | (5) |
|    | b) Explain the working of an RC coupled amplifier.      | (5) |

**OR**

- |    |  |     |
|----|--|-----|
| 20 | a) Describe the working of a zener diode voltage regulator.            | (5) |
|    | b) Draw and explain the frequency response of an RC coupled amplifier. | (5) |

**Module-VI**

- |    |  |     |
|----|--|-----|
| 21 | a) Draw the frequency spectrum of an amplitude modulated (AM) wave. Given that modulating signal is of frequency $f_m$ and amplitude $V_m$ and carrier is of frequency $f_c$ and amplitude $V_c$ . Take modulation index as $m$ . What is the bandwidth requirement of this AM wave? | (5) |
|    | b) With a neat sketch explain AM super heterodyne receiver.  | (5) |

**OR**

- |    |  |     |
|----|--|-----|
| 22 | a) Describe the principle and block diagram of a GSM system.                   | (5) |
|    | b) Explain the concept of cells and frequency reuse in cellular communication. | (5) |

\*\*\*\*\*